

SIMULATION AND IMPLEMENTATION OF COMBINATIONAL LOGIC CIRCUITS

AIM:

To simulate ENCODER, DECODER, MULTIPLEXER, DEMULTIPLEXER, MAGNITUDE COMPARATOR using VIVADO 2023.2.

APPARATUS REQUIRED:

VIVADO 2023.2

PROCEDURE:

STEP:1 Start the Xilinx navigator, Select and Name the New project.

STEP:2 Select the device family, device, package and speed.

STEP:3 Select new source in the New Project and select Verilog Module as the Source type.


STEP:4 Type the File Name and Click Next and then finish button. Type the code and save it.

STEP:5 Select the Behavioral Simulation in the Source Window and click the check syntax.

STEP:6 Click the simulation to simulate the program and give the inputs and verify the outputs as per the truth table.

ENCODER

LOGIC DIAGRAM

 


VERILOG CODE

```

module encoder(a,y);
input [7:0]a;
output[2:0]y;
or(y[2],a[6],a[5],a[4],a[3]);
or(y[1],a[6],a[5],a[2],a[1]);
or(y[0],a[6],a[4],a[2],a[0]);
endmodule


```

OUTPUT WAVEFORM

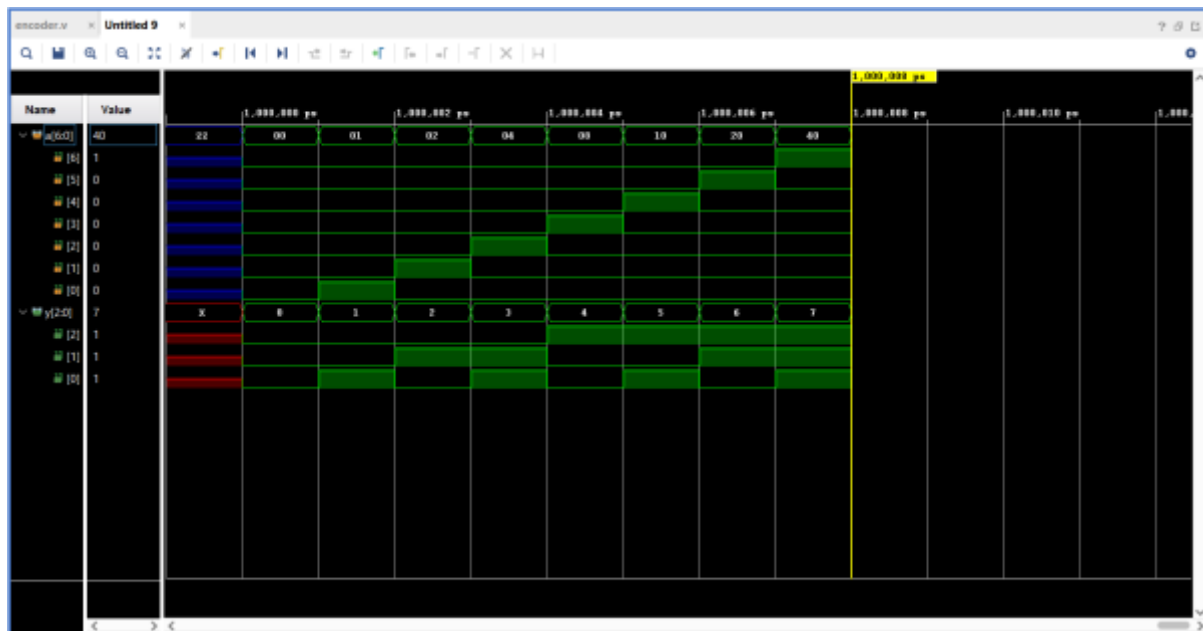

DECODER

LOGIC DIAGRAM

 


VERILOG CODE

```

module decoder1(a,y);
input [2:0]a;
output[7:0]y;
and(y[0],~a[2],~a[1],~a[0]);
and(y[1],~a[2],~a[1],a[0]);
and(y[2],~a[2],a[1],~a[0]);
and(y[3],~a[2],a[1],a[0]);
and(y[4],a[2],~a[1],~a[0]);
and(y[5],a[2],~a[1],a[0]);
and(y[6],a[2],a[1],~a[0]);
and(y[7],a[2],a[1],a[0]);
endmodule


```

OUTPUT WAVEFORM

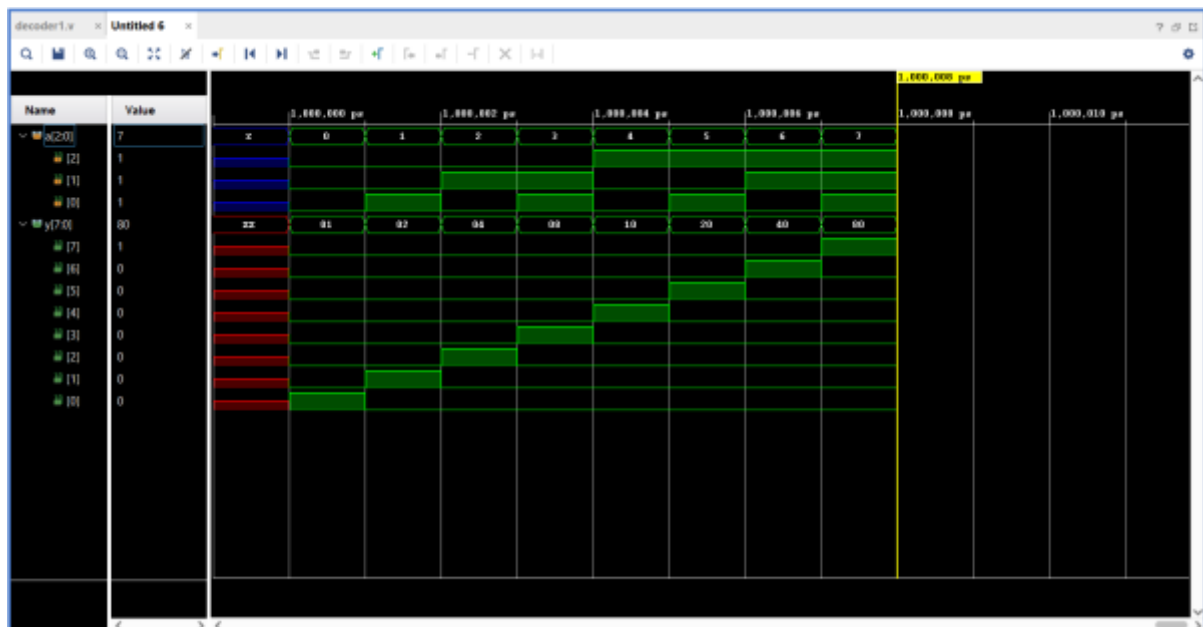

MULTIPLEXER

LOGIC DIAGRAM

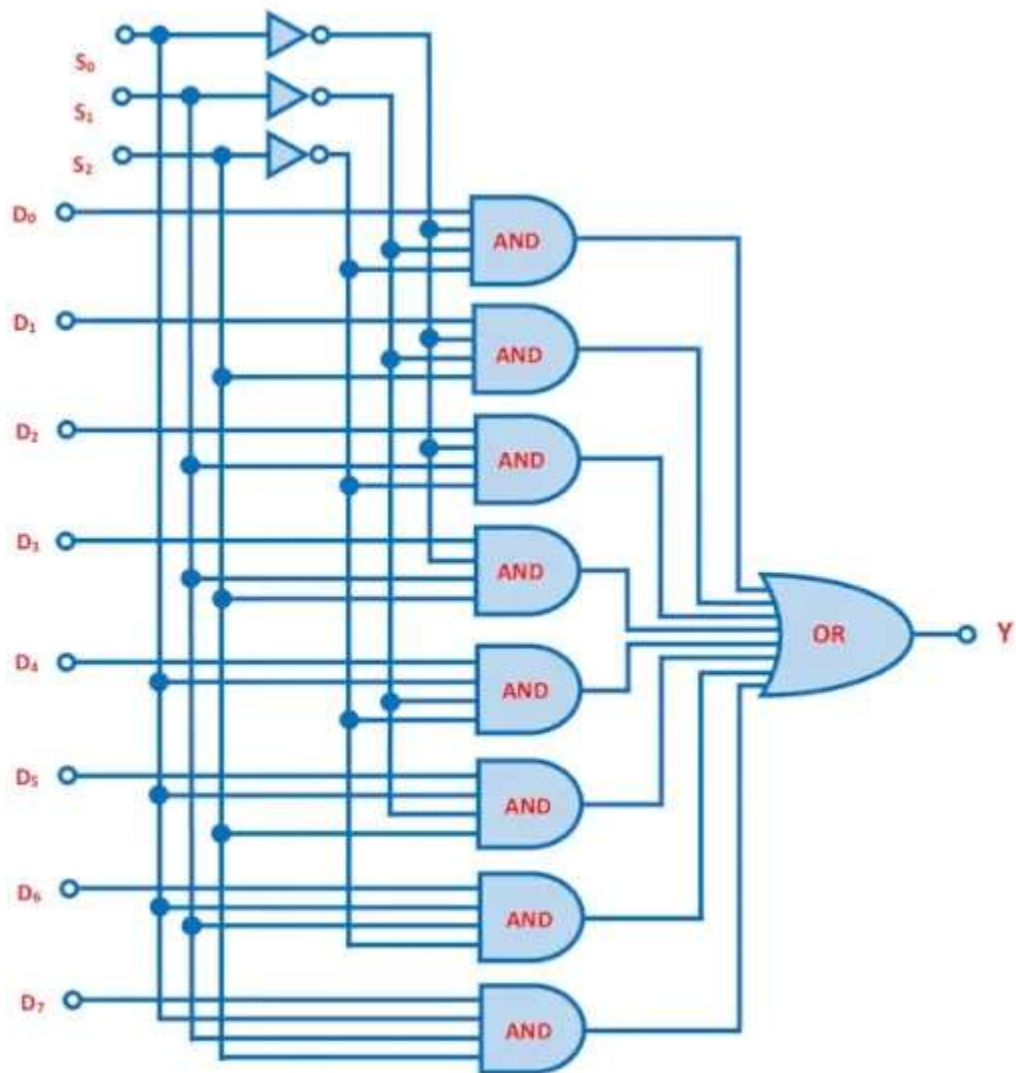

VERILOG CODE

```

module mux(s,c,a);
input [2:0]s;
input [7:0]a;
wire [7:0]w;
output c;
and(w[0],a[0],~s[2],~s[1],~s[0]);
and(w[1],a[1],~s[2],~s[1],s[0]);
and(w[2],a[2],~s[2],s[1],~s[0]);

```

```

and(w[3],a[3],~s[2],s[1],s[0]);
and(w[4],a[4],s[2],~s[1],~s[0]);
and(w[5],a[5],s[2],~s[1],s[0]);
and(w[6],a[6],s[2],s[1],~s[0]);
and(w[7],a[7],s[2],s[1],s[0]);
or(c,w[0],w[1],w[2],w[3],w[4],w[5],w[6],w[7]);
endmodule


```

OUTPUT WAVEFORM



DEMULTIPLEXER

LOGIC DIAGRAM

 

VERILOG CODE

```

module demux_8(s,a,y);
input [2:0]s;
input a;
output [7:0]y;
and(y[0],a,~s[2],~s[1],~s[0]);
and(y[1],a,~s[2],~s[1],s[0]);
and(y[2],a,~s[2],s[1],~s[0]);
and(y[3],a,~s[2],s[1],s[0]);
and(y[4],a,s[2],~s[1],~s[0]);
and(y[5],a,s[2],~s[1],s[0]);

```

```
and(y[6],a,s[2],s[1],~s[0]);
```

```
and(y[7],a,s[2],s[1],s[0]);
```

```
endmodule
```

OYTPUT WAVEFORM



MAGNITUDE COMPARATOR

LOGIC DIAGRAM



VERILOG CODE

```
module comparator(a,b,eq,lt,gt);
```

```
input [3:0] a,b;
```

```
output reg eq,lt,gt;
```

```
always @(a,b)
```


```
begin
```

```
if (a==b)
```



```
begin
    eq = 1'b1;
    lt = 1'b0;
    gt = 1'b0;
end
else if (a>b)
begin
    eq = 1'b0;
    lt = 1'b0;
    gt = 1'b1;
end
else
begin
    eq = 1'b0;
    lt = 1'b1;
    gt = 1'b0;
end
end
endmodule
```

OYTPUT WAVEFORM

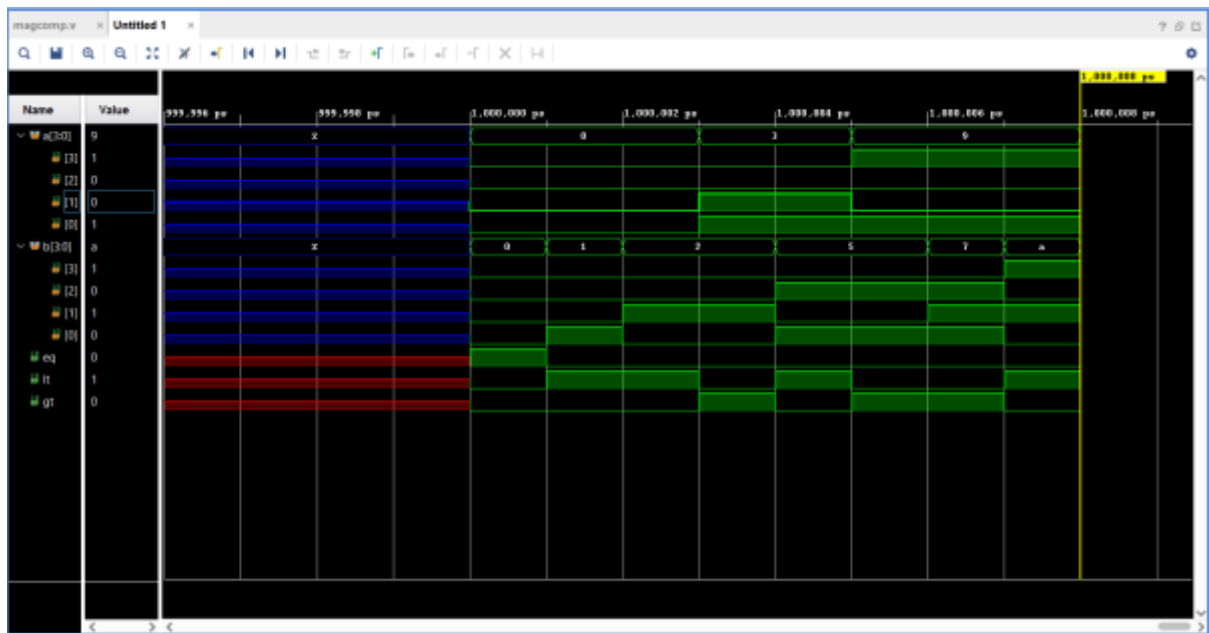

RESULT

Thus, the given encoder, decoder, multiplexer, demultiplexer, magnitude comparator are simulated successfully.